

How I Built My

Monsters In The Dark™ Eerie Monster Eyes™

This concept is so simple it is scary.
This design is for those that only want to build the scary best.
The dead have been “sticking” around to get one or two or three.

Warning
Build and Operate At Your Own Risk

Visit Us Online At

www.HalloweenPropShop.com

Please let us know if you find any grave errors in this document.
You can contact us via our web site.

This document may contain drawings created in color.
We recommend that you print this document in color.

If you have received this document in printed form and would like to receive this document **free of charge** in an electronic format then visit the [Halloween Prop Shop](http://www.Halloween Prop Shop) web site today.

© Copyright 2006 Ronald Yemmans II – All Rights Reserved
Monsters In The Dark™ and Eerie Monster Eyes™ Trademarks
Are the property of Ronald Yemmans II

Table of Contents

Suppliers	3
Component Pictures.....	4
Recommended Tools	5
Introduction	7
Terms You Need To Know	8
LED Brightness.....	8
LED Sizes.....	8
LED Operating Voltages	8
LED Operating Currents	8
LED Viewing Angles	8
LED Data Sheet Information.....	8
How does it work?	9
Connecting 2 LED's in series.....	9
Single Pair of Light Emitting Diodes.....	10
Calculating the Resistor Value.....	11
Two Pair of Light Emitting Diodes.....	13
Five Pair Circuits Compared.....	15
Assembly Guidelines.....	16
Trouble "Shooting".....	17
Disclaimer	18
Distribution Terms and Conditions	20

Suppliers

Radio Shack – www.radioshack.com

I would like to note that Radio Shack is not the least expensive place to purchase your components. I have chosen to use their part numbers as Radio Shack is a nation wide chain of stores that you can quickly run to and pick up the parts.

Specifications and prices are subject to change and are as of July, 2006

The wiring diagrams in this document show 6 volt batteries. The parts list calls out 9 volt components. Feel free to double check the math for the resistor value.

Generic LED Eyes Parts List Makes 5 Pair Of LED Eyes In Single Project Box

QTY Required	Description	Part Number	Price Per Unit	Project Cost
10	Bright RED Diffused Lens LED	276-330	\$1.39	\$13.90
1	270 Ohm - 1/2W Resistors	271-1112	\$0.99	\$0.99
1	9V Battery Clip	270-324	\$2.59	\$2.59
1	Plastic Enclosure	270-1803	\$3.69	\$3.69
1	Heat Shrink Tube	278-1627	\$2.99	\$2.99
1	Mini Toggle Switch	275-645	\$2.99	\$2.99
1	Hook Up Wire	278-1224	\$5.99	\$5.99
Total				\$33.14

If you purchase 4 more project boxes you can spread your LED eyes out and each will cost less than \$9.00 to build.

The Halloween Prop Shop – www.HalloweenPropShop.com

If you are having problems find parts or want a better selection then contact me and I may be able to help.

Component Pictures

Typical Representations

	Battery Clip for 9V battery
	Resistors ¼ watt and ½ watt
	Light emitting diode or LED
	The project box will hold the battery, battery clip and resistor. A hole will be drilled to allow the wires to go to the LED's and for the optional toggle switch to be mounted.
	Toggle switch will be used to turn power on and off to the Light Emitting Diodes.
	Hook up wire will be used to connect the parts together.
	Heat shrink tube will be used to insulate the solder joints and component leads

Recommended Tools



If you are going to be doing your own electronics project then I strongly recommend that you purchase a quality soldering station and not a \$20.00 (or less) piece of junk. Also get a solder holder; it makes life so much easier.

This clip on heat sink is used to protect the device you are soldering. The heat from a soldering iron can destroy the part you are soldering if you let it over heat the part. By clipping this heat sink (on the part lead) between the part and soldering iron it will “help” prevent damaging your part. I recommend you get 2 or 3 of these.



Wire strippers are used to strip the insulation off your wire. Higher quality strippers have notched areas for different sized wires plus a regular cutting blade.



Quality Mini-Pliers & Cutter set.



Quality Screw Driver Set.



The drill will be used for drilling the holes for the wires and toggle switch in the enclosure.





Glue gun for gluing the wires and resistor in the enclosure. The wires are glued to help prevent them from being pulled out of the box.



Heat shrink gun with the proper attachment and heat shrink tubing can be used to insulate solder joints and component leads.



Loctite™ is used to keep nut from coming loose on bolts or in our case, the toggle switch nut. You will need this if you install the optional toggle switch.

Introduction

Monster Eyes are a great way to add a little spookiness to your haunt. They can be placed in bushes, in a hallowed out tree, near the ground, embedded in a tombstones and masks and even in the eyes of Owl hunting decoys.

What are Monster Eyes? These are 2 light emitting diodes (LED) that are connected to power supply or set of batteries. Place 2 LED's a few inches apart from each other and in a dark area and it looks as if a creature of some type is staring at you. Place a few pairs of Monster Eyes on the roof and around your cemetery and you can create a really eerie effect.

First, lets starts out by saying there are many different sizes, colors, and levels of brightness that you can choose from when it comes to picking out what type of LED's you want to use. LED's also come in clear and diffused cases as well as several viewing angles.

When it comes to price you will find LED's in retail stores typically ranging from 65 cents a piece to several dollars each.

Terms You Need To Know

LED Brightness - Typically rated in mcd, the higher the brighter.

LED Sizes - Typically 3mm, 5mm, 8mm, and 10mm

LED Operating Voltages - Typically called out on data sheets as Voltage Forward (Vf). Most common LED's operate in the 1.9 volt to 2.2 volt range. With the addition of new colors and levels of brightness you must look up the Forward Voltage rating of your LED's on the manufacturer's data Sheet.

LED Operating Currents - Typically called out on a data sheet as Forward Current (If). Most common LED's operate in the 17mA to 25mA range. With the addition of new colors and levels of brightness you must look up the Forward Voltage rating of your LED's on the manufacturer's data sheet.

LED Viewing Angles - Is how wide the beam is when the light leaves the LED. Typically, the narrower the viewing angle the brighter the LED will be when compared to the same type of LED with a wide viewing angle.


LED Data Sheet Information

Electrical / Optical Characteristics at TA=25°C

Symbol	Parameter	Device	Typ.	Max.	Units	Test Conditions
λ_{peak}	Peak Wavelength	Hyper Red	650		nm	If=20mA
λ_D	Dominant Wavelength	Hyper Red	635		nm	If=20mA
$\Delta\lambda_{1/2}$	Spectral Line Half-width	Hyper Red	28		nm	If=20mA
C	Capacitance	Hyper Red	35		pF	Vf=0V;f=1MHz
V_F	Forward Voltage	Hyper Red	1.95	2.5	V	If=20mA
I _R	Reverse Current	Hyper Red		10	uA	V _R = 5V

How does it work?

Connecting 2 LED's in series

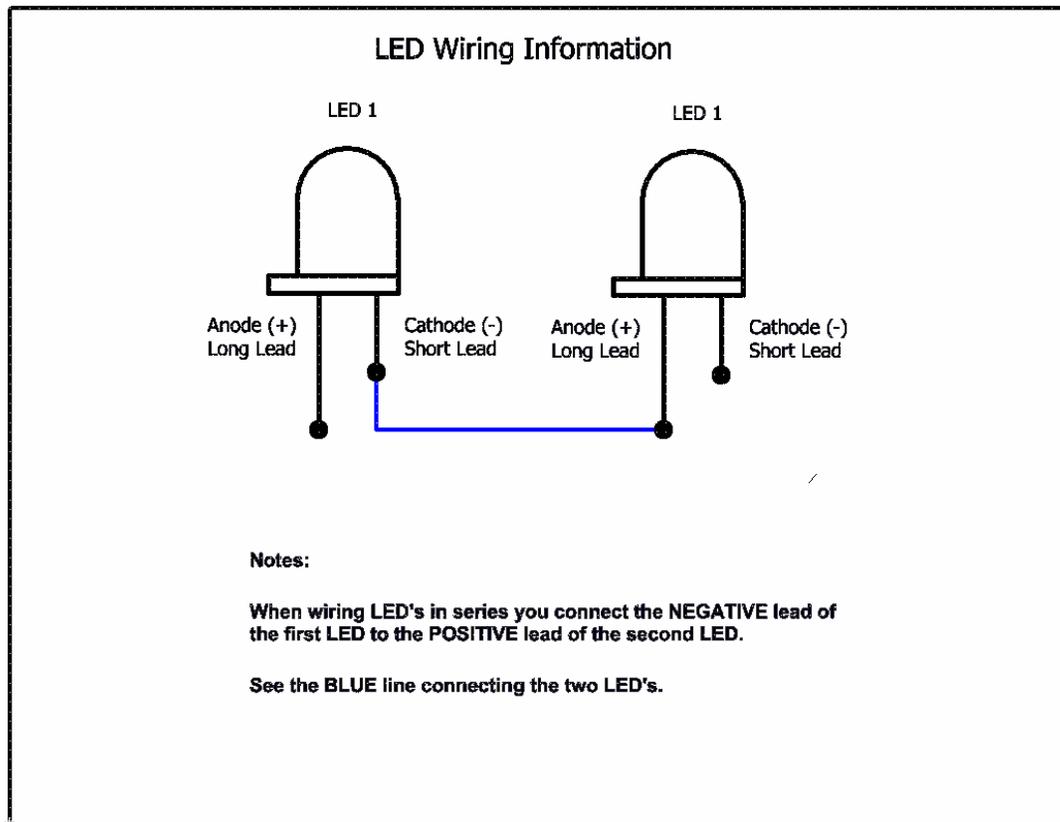

When connecting two LED's in series it is important to connect them properly. If you do not wire the LED's properly they will not light up and you might damage both LED's.


In most cases the long lead of the LED will be the Anode or positive lead and the short lead will be the cathode or negative lead. To properly connect two LED's in series you connect the **SHORT** lead of the first LED to the **LONG** lead of the second LED.

WARNING – I have found a few LED's that operate in the opposite manner. You should always read the data sheet of the LED's before connecting them to a circuit.

Single Pair of Light Emitting Diodes

The drawing below is a very simply “series” circuit. The batteries are connected in series to supply 6 VDC to the electronic components. The electronic components consist of a single resistor and two light emitting diodes all wired in series.

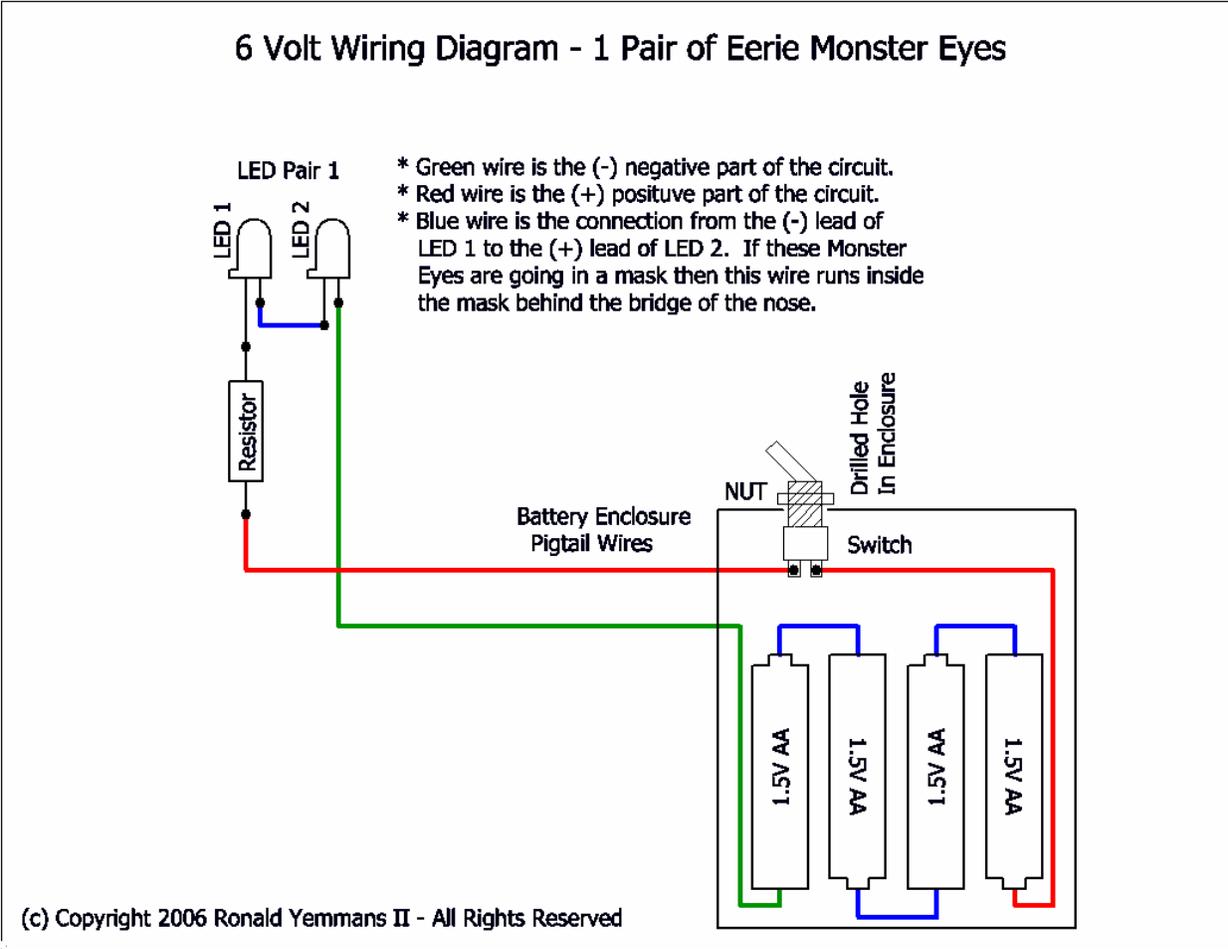When you first apply power to a light emitting diode, the LED draws a very high amount of current. The circuit will draw too much current from the batteries and will destroy the LED. By placing a resistor (value must be calculated) in series with an LED(s) the amount of current drawn from the batteries will be limited and will prevent the LED from being damaging.



Calculating the Resistor Value

First you need to read the data sheet for the LED's you have chosen to use. There is two specifications you are most interested. The first specification is the operating voltage range of the light emitting diodes. The second specification is the maximum operating current allowed.


Example 1

LED Specifications:

Operating Voltage Range 1.9VDC – 2.1 VDC

Maximum Operating Current 20mA or **.020 Amps**

Battery Pack Used 6VDC

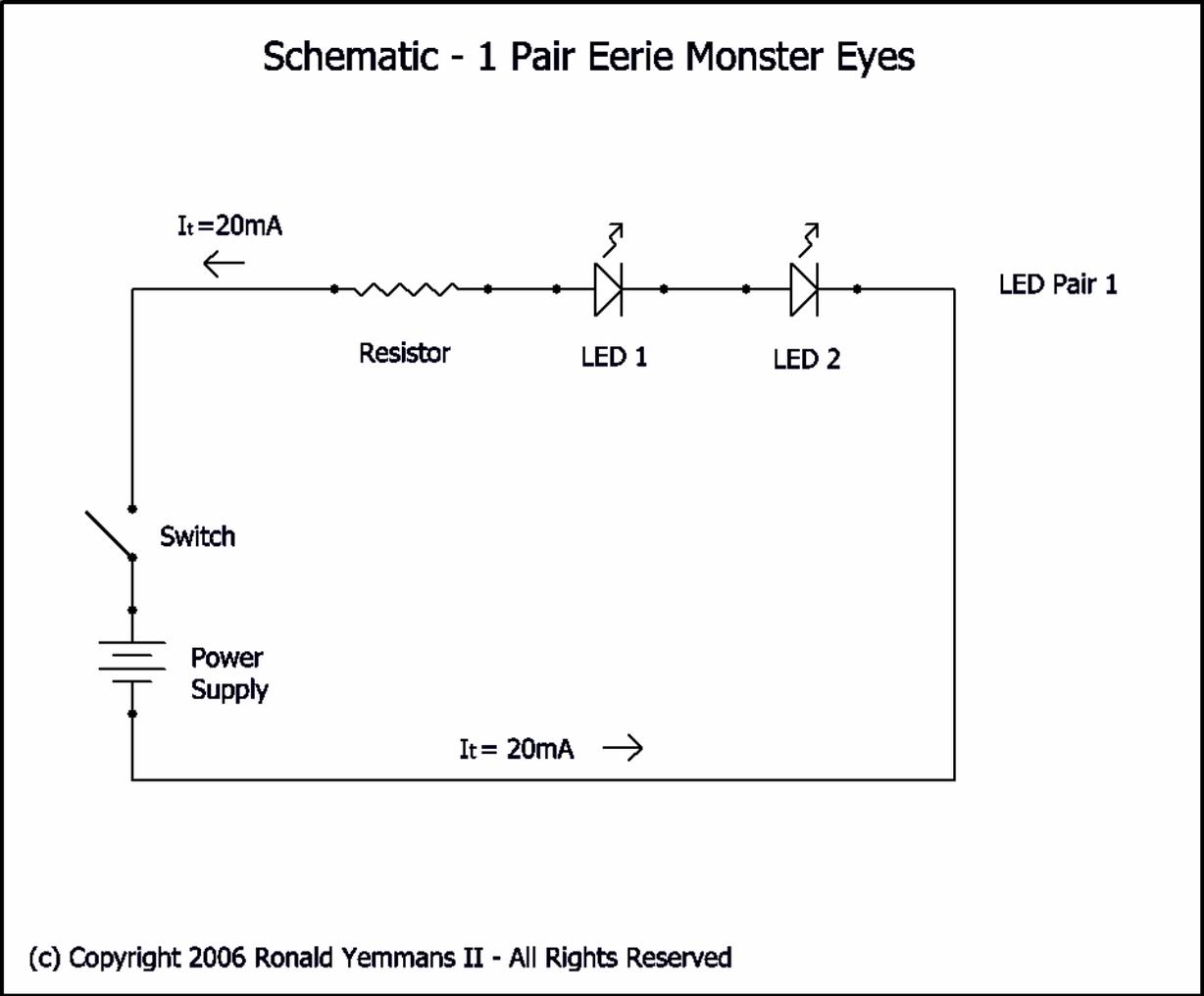

Step 1 – Calculate the voltage used by the resistor.

All the components on a circuit will use up the total voltage supplied by the batteries. Since the LED's we have chosen to use are identical they will use the same amount of voltage. We need to calculate how much voltage the resistor will then use.

Since all three components are wired in series you simply add the voltages used together.

$$\text{Battery} = \text{Resistor} + \text{LED 1} + \text{LED 2} \quad 6 \text{ VDC} = \mathbf{X \text{ VDC}} + 2.1 \text{ VDC} + 2.1 \text{ VDC}$$

$$\text{Algebra – YUK!} \quad 6\text{VDC} - 2.1 \text{ VDC} - 2.1\text{VDC} = \mathbf{1.8 \text{ VDC}}$$

1.8 VDC is how much voltage the resistor must use.

Step 2 – Calculate the resistance value of the resistor.

Now that we know how much voltage the resistor needs to use up AND we know that the maximum current allowed through the LED's we can calculate the resistor value in ohms.

$$\text{Resistance} = \text{Voltage} / \text{Current} \quad = \mathbf{1.8 \text{ VDC} / .020 \text{ Amps} = 90 \text{ Ohms}}$$

Note: If you cannot find a 90 Ohms resistor then use the next **LARGER** size (90 – 110 ohms)

Step 3 – Calculate the **minimum** power rating of the resistor.

When the resistor uses up the **1.8 VDC** heat will be generated. If you pick to low a power rating the resistor will burn up.

$$\text{Power} = \text{Current} \times \text{Voltage} \quad = \mathbf{.020 \text{ Amps} \times 1.8\text{VDC} = .036 \text{ Watts}}$$


You will see that the most common power ratings for resistors are 1/8, 1/4, and 1/2 Watts.

1/8 Watts = **.125 Watts**, since this is a much higher rating than we calculated (**.036 Watts**) we should be safe.

The resistor required for the above circuit is **90 Ohm, 1/8 Watt**.

Two Pair of Light Emitting Diodes

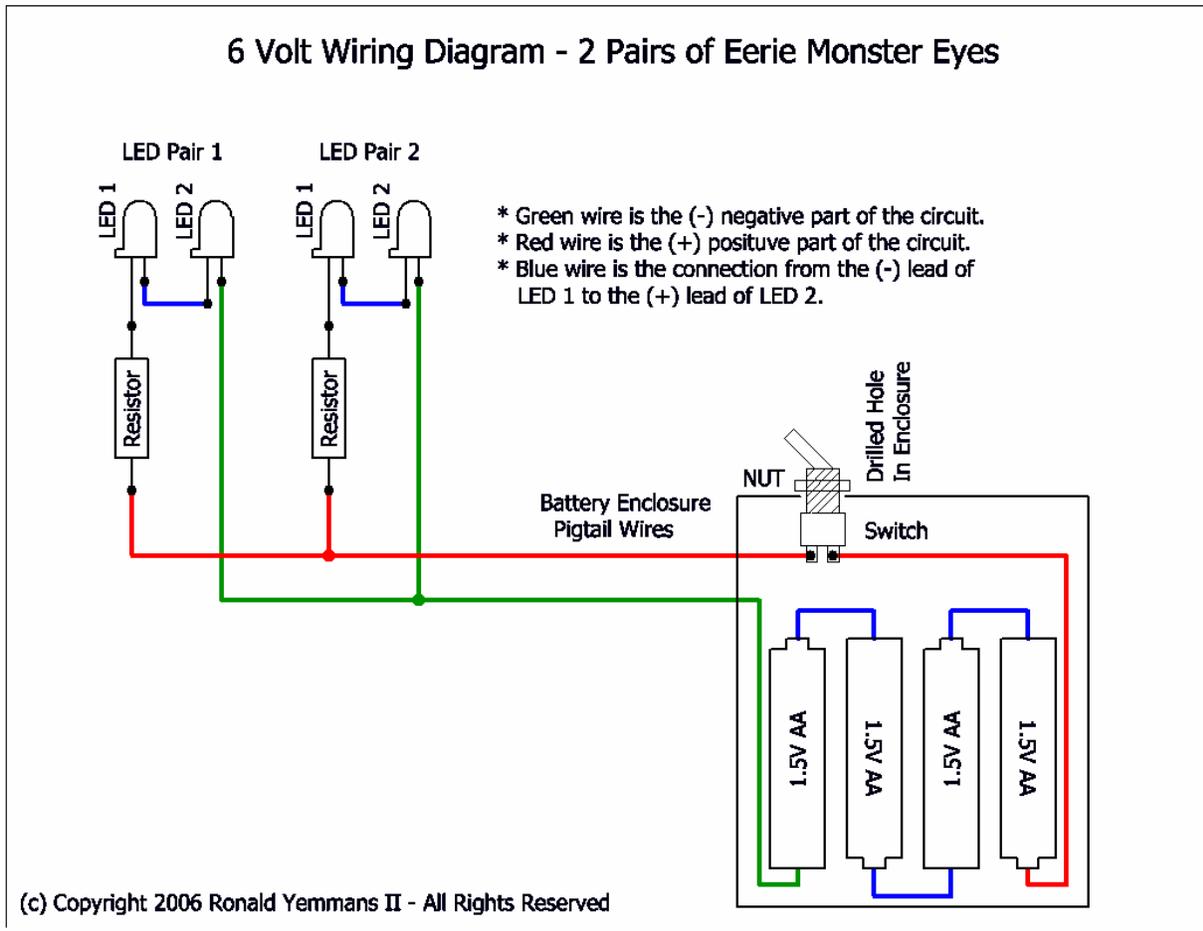If you take a moment to look at this circuit you will notice that each pair of LED's is wired EXACTLY the same as Example 1. When we add the second pair to the circuit as shown below we call it a "parallel" circuit, meaning that each "set" of eyes are wired parallel to each other.



Is there a difference in how this circuit works as compared to the circuit in Example 1? Only a minor difference exists. This difference is that a total of **.040 amps** will be drawn from the batteries which will cause them to "die" twice as fast.


LED Pair 1 will draw a total of **.020 amps**

LED Pair 2 will draw a total of **.020 amps**

All other aspects of the circuit remain the same as in Example 1.

If you want to learn more then search the WWW for Ohms law.



Schematic - 2 Pair Eerie Monster Eyes

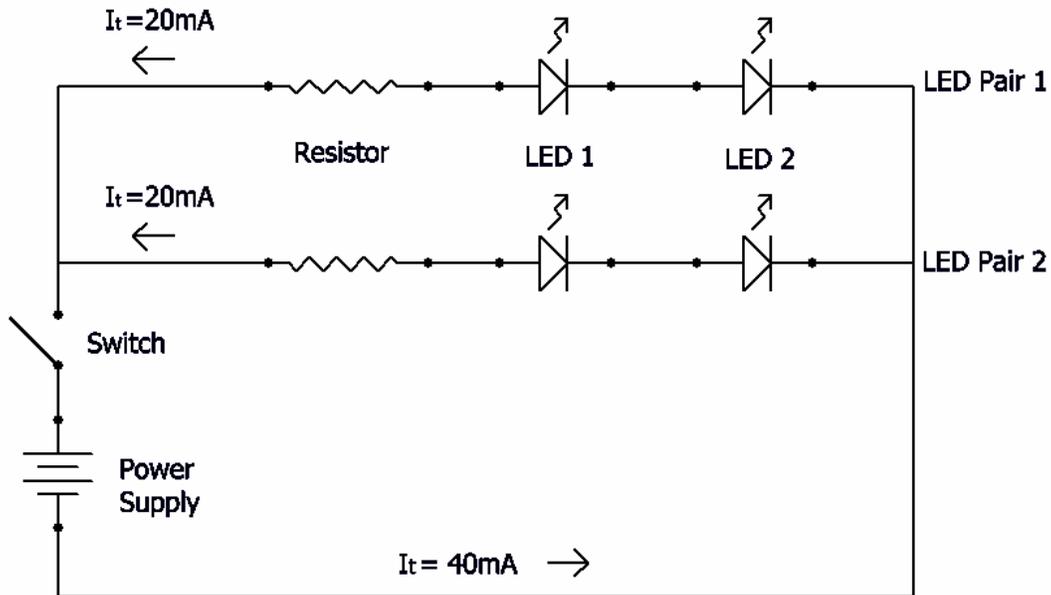

(c) Copyright 2006 Ronald Yemmans II - All Rights Reserved

Note: Some of you may have noticed that the arrows showing current flow are pointing towards the positive side of the battery. Current flow is actually the flow of electrons. Electrons are negatively charged particles and are attracted to the positive end of the battery. While many people believe that “electricity” flows positive to negative this is not the case.

Five Pair Circuits Compared

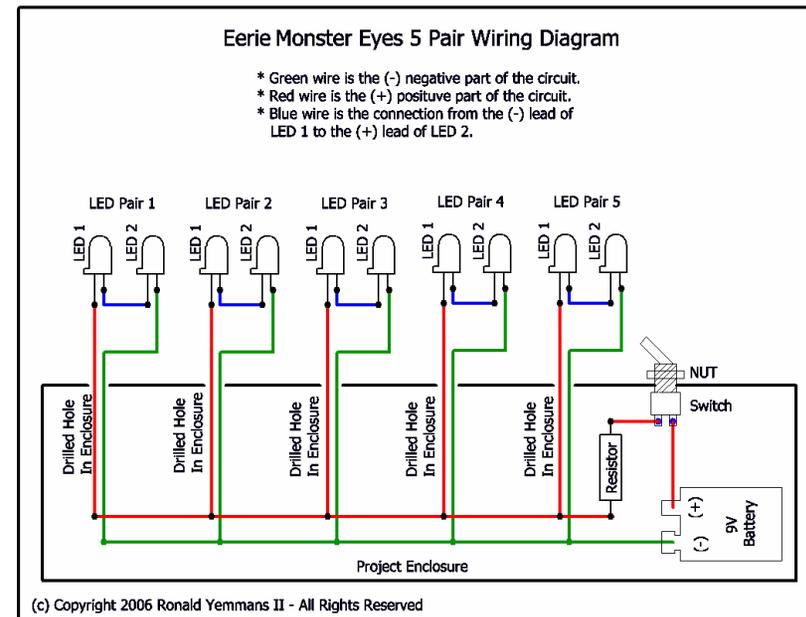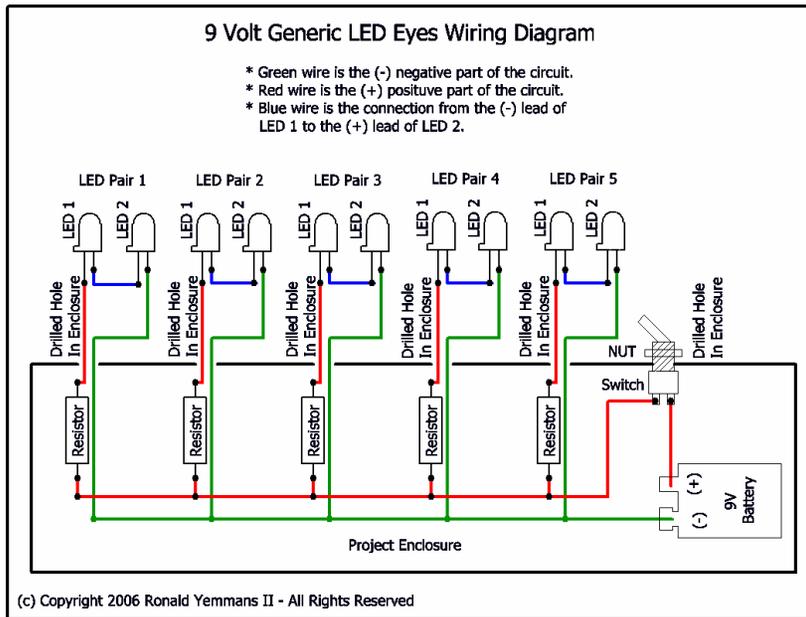

Note: These two circuits are functionally the same. The second circuit reduces the number of number of resistors from 5 down to 1. The important thing to realize here is that considerably more current is flowing through the single resistor and we need to be concerned with the **HEAT** that will build up in it.

Recalculate power requirement for a single resistor.

.020 Amps per set of eyes
Power = Voltage x Current

.020 Amps x 5 sets = **.100 Amps**
1.8 VDC x .100 Amps = **.180 Watts**

The minimum power rating for the single resistor should be no smaller the ¼ Watt, you might even consider using a ½ Watt resistor just to be safe.

© Copyright 2006 Ronald Yemmans II – All Rights Reserved
Monsters In The Dark™ and Eerie Monster Eyes™ Trademarks
Are the property of Ronald Yemmans II

Assembly Guidelines

The following assembly guidelines are for construction of the 6 volt circuit with a single pair of LED's in example 1.

1. Remove the face plate/cover from the enclosure.
2. Drill the mounting hole in the face plate/cover for the toggle switch you purchased.
3. Drill a small hole in the face plate/cover for the wires to come out and run to the LED's.
4. Solder all the components together as shown in the diagram of Example 1.

Remember to use your heat sink to protect your LED's from the heat.

You must confirm that the positive leg of the LED's you are using is the long leg on your LED's.

Cover all exposed solder joints with heat shrink tubing.

5. Assembly the box as shown in the 9 Volt 5 LED eyes Example. If you install all 5 pairs of LED's then purchase a little larger project box so all the resistors will fit inside. You should use heat shrink tube to prevent the resistor leads from short circuiting out the unit.
6. Install your battery and test the unit.

Trouble “Shooting”

If the LED's do not come on it is most likely due to one of the following reasons.

1. You took too long to solder the LED's and you damaged one or both. Read the data sheet for the LED's you have chosen. They specify how long you can apply the heat to an LED before you burn it out. Using a clamp on heat sink can help delay any damage due to heat. You typically have less than 2 seconds to hand solder LED's with a low wattage soldering iron.
2. You have the battery leads connected backwards in the circuit. This could damage the LED's.
3. You soldered one of the LED's into the circuit backwards.
4. You miscalculated the resistance value of the resistor and used up too much voltage at the resistor. This should not damage the LED's.
5. You miscalculated the resistance value of the resistor and did not use up enough of the voltage from the battery. This would damage the LED's.
6. You miscalculated the resistance value of the resistor and are drawing too little current from the batteries. This should not damage the LED's.
7. You miscalculated the resistance value of the resistor and are drawing too much current from the batteries. This would damage the LED's.

I call it trouble “Shooting” because if most of the reasons listed above will burn out the LED's and there is no way to fix them. So you “shot” yourself in the foot.

If you want to practice soldering cheap LED's before using your really good ones then look for some low power cheapies.

Disclaimer

1. The information obtained from within this document and/or web site is provided "AS IS", without warranty, expressed or implied, as to the merchantability or fitness for any purpose.
2. The reader(s) and/or user(s) acknowledge that the information obtained from within this document and/or web site is to be considered experimental and potentially dangerous to people that have not been professionally trained to handle such information and/or equipment described within said document and/or web site.
3. Any person(s) reading and/or using the information obtained from this document and/or web site accepts full responsibility and all liability for any outcomes expected or unexpected that may occur while using said information including but not limited to, the equipment used in the construction of produced object(s), or the operation of the constructed object(s).
4. Any person(s) reading and/or using the information obtained from this document and/or web site agrees that he/she/they shall hold harmless including but not limited to; Ronald Yemmans II, the Halloweenpropshop.com web site and it's affiliates, and all authorized distributors for any and all damages that may occur while using enclosed information or the resulting tangible equipment produced.
5. Any person(s) reading and/or using the information obtained from this document and/or web site agrees to hire a professional engineering company to evaluate and make all necessary modifications to this information to satisfy his/her/their requirements.
6. In the event that the readers and/or users local and state laws do not provide for such limitations as stated above then the reader and/or user agrees that any and all legal action taken will be pursued in the state in which Ronald Yemmans II resides in at the time of said legal action and that the maximum financial liability shall not exceed the original purchase price paid directly to Ronald Yemmans II for said information.
7. The information contained within the document is subject to change without notice.
8. The Halloween Prop Shop is not responsible for any errors that may be found in this document and/or web site.
9. Reading and/or using the information contained within this document and/or web site constitutes acceptance of the Disclaimer Terms and Conditions.

© Copyright 2006 Ronald Yemmans II – All Rights Reserved
Monsters In The Dark™ and Eerie Monster Eyes™ Trademarks
Are the property of Ronald Yemmans II

Distribution Terms and Conditions

1. This document may only be distributed in its original, unedited form.
2. This document must be distributed **FREE OF CHARGE**.
3. This document may not be distributed as an incentive to try and/or purchase a service, membership, or product.
4. This document may only be distributed by authorized companies, organizations, clubs or individuals.
5. Those companies, organizations, clubs or individuals that have been authorized to distribute this document will receive a non-exclusive license at no charge/cost to distribute this document and said license may be cancelled/revoked at any time by Ronald Yemmans II and/or the [Halloween Prop Shop](#) without cause and/or reason.
6. Those companies, organizations, clubs or individuals wishing to distribute this document must contact the [Halloween Prop Shop](#) and receive written permission prior to distributing said information, and must renew their non-exclusive license on or before November 15 for the following calendar year (January 1 – December 31).

Example: To distribute this document from January 1, 2000 through December 31, 2000 the application must be submitted no later than November 15, 1999.

7. All distribution licenses automatically expire on December 31 of each year.
8. Typical distribution methods including, but not limited to, web site downloads, electronic mail and/or physical media such as a printed copy, CD/DVD ROM/RAM Discs or flash memory drives and cards are acceptable to the [Halloween Prop Shop](#).
9. Electronic distribution must be done directly from the distributing entity's servers/computers/accounts and not via the web servers of the [Halloween Prop Shop](#).
10. Physical media distribution such as printed/paper media may include the distributing entity's name, as received on the distribution application. Physical media distribution such as, CD/DVD ROM/RAM Discs or similar must have the [Halloween Prop Shop](#) full web site Universal Resource Locator (URL) clearly printed and easily viewable in the font size of not less than 12 point printed directly on the visible media surface and/or label placed on the media surface.

11. The “Distribution Terms and Conditions” are subject to change without notice.
12. Applying for an authorized distribution license constitutes acceptance of the “Distribution Terms and Conditions”.